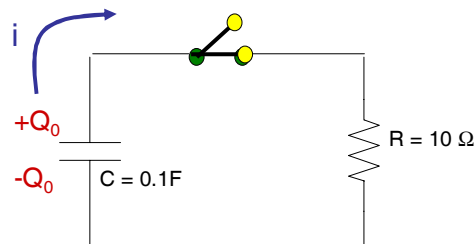



RC circuits

Initially one has $+Q_0$ and $-Q_0$ on the Capacitor plates.
Thus, the initial Voltage on the Capacitor $V_0 = Q_0/C$.
What do you think happens when the switch is closed?



Discharging a capacitor

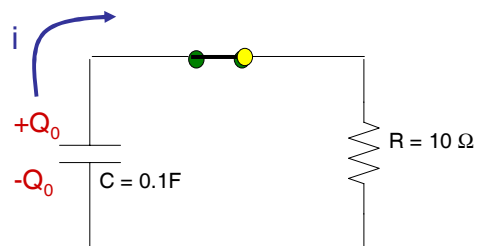Close the switch at $t=0$, then current i starts to flow.




$$\text{At } t=0, \quad i_0 = \frac{V_0}{R}$$

$$\text{Later } i(t) = -\frac{dQ}{dt}$$

* Negative sign since Q is decreasing.

Discharging a capacitor

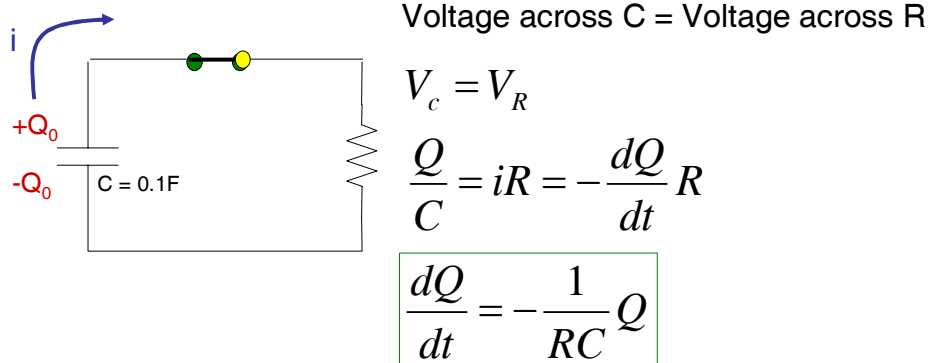

We now need to solve this differential equation.

Discharging a capacitor

Solving the differential equation:

$$\frac{dQ}{dt} = -\frac{1}{RC} Q \longrightarrow Q(t) = Q_0 e^{-t/RC}$$

Check solution by taking the derivative...


$$\frac{dQ}{dt} = Q_0 \left(-\frac{1}{RC} \right) e^{-t/RC} = -\frac{1}{RC} Q$$

Also $Q(t) = Q_0$ at $t=0$. $Q(t=0) = Q_0 e^{-0/RC} = Q_0$

Discharging a capacitor

Exponential Decay

$$Q(t) = Q_0 e^{-t/RC}$$

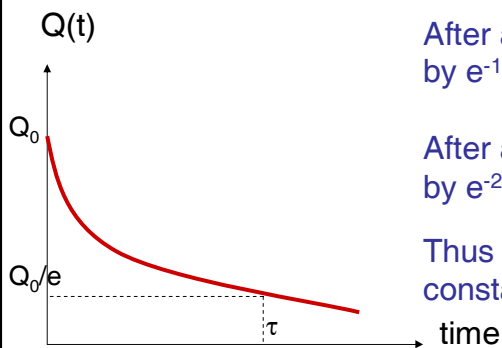

After a time $\tau = RC$, Q has dropped by $e^{-1} = 1/e$.

After a time $t = 2RC$, Q has dropped by $e^{-2} = 1/e^2$

Thus $\tau=RC$ is often called the time constant and has units [seconds].

Discharging a capacitor

$$\frac{dQ}{dt} = Q_0 \left(-\frac{1}{RC} \right) e^{-t/RC} = -\frac{1}{RC} Q$$

$$|i(t)| = \left| \frac{dQ}{dt} \right| = \left(\frac{Q_0}{RC} \right) e^{-t/RC} = i_0 e^{-t/RC}$$

Thus, the current also falls with the same exponential function.

Clicker Question

A capacitor with capacitance 0.1F in an RC circuit is initially charged up to an initial voltage of $V_0 = 10\text{V}$ and is then discharged through an $R=10\Omega$ resistor as shown. The switch is closed at time $t=0$. Immediately after the switch is closed, the initial current is $I_0 = V_0 / R = 10\text{V} / 10\Omega$.

What is the current I through the resistor at time $t=2.0\text{ s}$?


A) 1A

C) $1/e\text{ A} = 0.37\text{A}$

E) None of these.


B) 0.5A

D) $1/e^2\text{ A} = 0.14\text{A}$

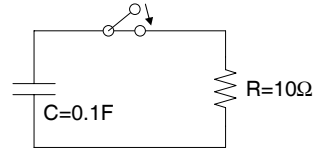

Charging a capacitor

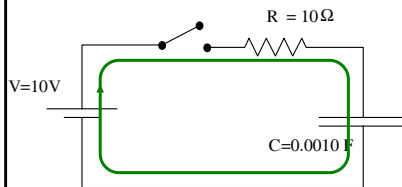More complex RC circuit: Charging C with a battery.



Before switch closed $i=0$, and charge on capacitor $Q=0$.

Close switch at $t=0$.

Try Voltage loop rule.

$$+V_b + V_R + V_C = 0$$

$$+V_b - iR - Q/C = 0$$

Charging a capacitor

$$+V_b - iR - Q/C = 0$$




$$+V_b - \frac{dQ}{dt} R - Q/C = 0$$

$$\frac{dQ}{dt} = +\frac{V_b}{R} - \frac{Q}{RC} \longrightarrow Q(t) = CV_b(1 - e^{-t/RC})$$

Charging a capacitor

$$Q(t) = CV_b(1 - e^{-t/RC})$$
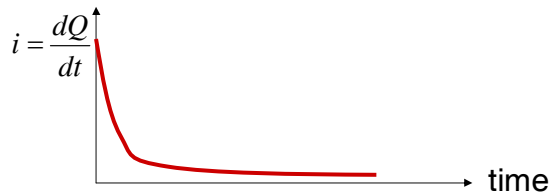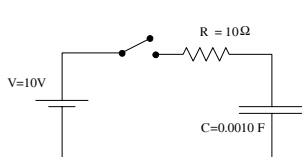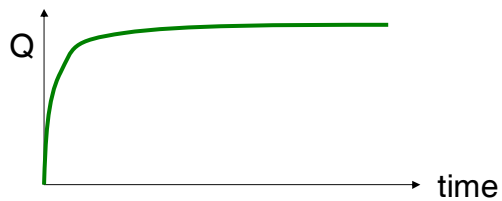
$$i(t) = \frac{dQ}{dt}(t) = \frac{V_b}{R} e^{-t/RC}$$



- Although no charge actually passes between the capacitor plates, it acts just like a current is flowing through it.
- Uncharged capacitors act like a “short”: $V_C = Q/C = 0$
- Fully charged capacitors act like an “open circuit”. Must have $i_C = 0$ eventually, otherwise $Q \rightarrow \text{infinity}$.

Clicker Question

An RC circuit is shown below. Initially the switch is open and the capacitor has no charge. At time $t=0$, the switch is closed. What is the voltage across the capacitor *immediately* after the switch is closed (time = 0)?

- A) Zero
- B) 10 V
- C) 5V
- D) None of these.

